

Lab 6 Cascaded C.E. Amplifiers

Name _____

Section _____

Purpose:

To demonstrate the ac operation of a two-stage (CE) amplifier.

Equipment:

- 1 dc Power Supply
- 1 Digital Multimeter (DMM)
- 1 Variable ac Signal Generator
- 1 Dual Trace Oscilloscope
- 2 2N3904 npn Transistors

Resistors

- | | |
|--------------------|--------------------|
| 2 - 150 Ω | 2 - 2.2 k Ω |
| 2 - 1 k Ω | 2 - 3.6 k Ω |
| 1 - 1.5 k Ω | 3 - 10 k Ω |

Capacitors

- | | |
|----------------|-----------------|
| 1 - 1 μ F | 2 - 470 μ F |
| 2 - 10 μ F | |

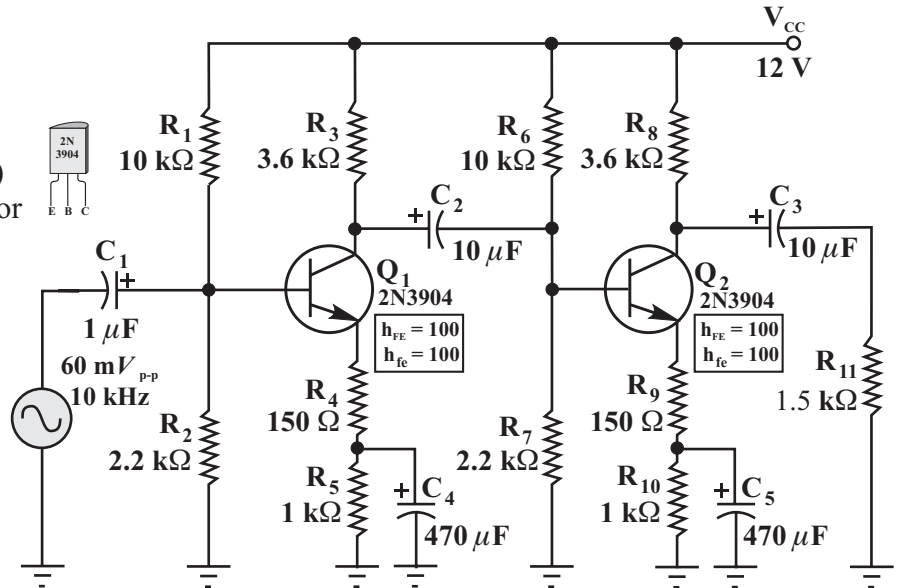


Figure 1

Prelab:

- Construct the circuit shown in Figure 1 on your breadboard.
- Perform the dc analysis for both stages and record your answers in the Table 1.

Show all calculations.

- Perform the ac analysis for both stages and record your answers in Table 2. The worksheet on ac analysis will take you step-by-step through the process.


Show all your calculations.

Discussion:

The amplified signal out of a CE stage can be used as the input to another CE stage. We know that the ordinary gains of each stage multiply. By building a multi-stage amplifier, we can achieve a very large voltage gain.

We know that a CE amplifier has an input impedance. Because this input impedance is the load for the preceding stage, it has a loading effect on the preceding stage. In other words, the loaded voltage gain is less than the unloaded voltage gain.

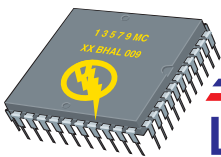In this lab, you will build a two-stage amplifier that uses swamped stages to stabilize the overall voltage gain.



Lab 6 Cascaded C.E. Amplifiers

- You found r'_e for stage 1 when you did the dc analysis. Use it now to find A_v . In this case r_e is the emitter resistor that is not bypassed, – the $150\ \Omega$ -- R_4

$$A_v = \frac{r_c}{r_e + r'_e}$$

$$A_{v1} = \text{_____} \text{ for stage 1}$$

- Find A_{v2}

Find r_c for stage 2. This is $R_c \parallel R_L$, so here it is $R_8 \parallel R_{11}$

$$r_c = \text{_____}$$

- Now find A_v for stage 2.

In this case r_e is the emitter resistor that is not bypassed, – the $150\ \Omega$ -- R_9

$$A_v = \frac{r_c}{r_e + r'_e}$$

$$A_{v2} = \text{_____} \text{ for stage 2}$$

- Find A_{VT} Ordinary gains multiply.

$$A_{VT} = (A_{v1})(A_{v2})$$

$$A_{VT} = \text{_____}$$

- Finding the ac terminal voltages V_B and V_C

$V_{B(Q1)}$ is at 60 mV_{p-p} since the generator is connected directly to it through capacitor C_1 . All capacitors in this amplifier are operating well above $10f_c$ and appear as short circuits to the ac signal.

$$V_{C(Q1)}$$
 is the amplified result of Q_1 . The formula $V_{out} = A_v V_{in}$ becomes $V_{C(Q1)} = A_{v(Q1)} V_{B(Q1)}$ $V_{C(Q1)} = \text{_____}$

$V_{B(Q2)}$ is at the same ac potential as $V_{C(Q1)}$ since there is a direct ac connection between them through capacitor C_2 . This capacitor is operating well above $10f_c$ and appears as a short circuit to the ac signal.

$$V_{C(Q2)}$$
 is the amplified result of Q_2 . The formula $V_{out} = A_v V_{in}$ becomes $V_{C(Q2)} = A_{v(Q2)} V_{B(Q2)}$ $V_{C(Q2)} = \text{_____}$


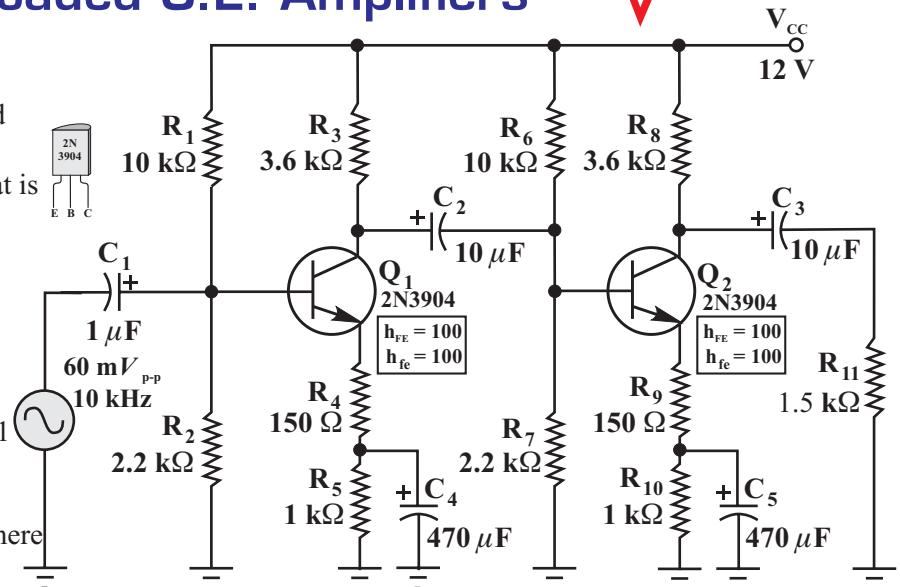
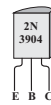


Figure 1

Table 2 ac Values	$A_{V(Q1)}$	$A_{V(Q2)}$	$A_{V(T)}$	$V_{B(Q1)}$	$V_{C(Q1)}$	$V_{B(Q2)}$	$V_{C(Q2)}$
Calculated							
Measured							

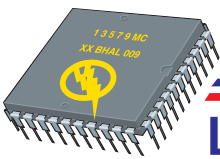

Lab 6 Cascaded C.E. Amplifiers

Procedure: Do this part in the Lab.

- 1) Measure and record the dc values shown in Table 1. Do this with the signal generator **disconnected** from the circuit.
- 2) Connect the signal generator to the circuit and set the output to **60 mV_{p-p}** using an oscilloscope.
- 3) Measure and record the ac values shown in Table 2 using the oscilloscope.

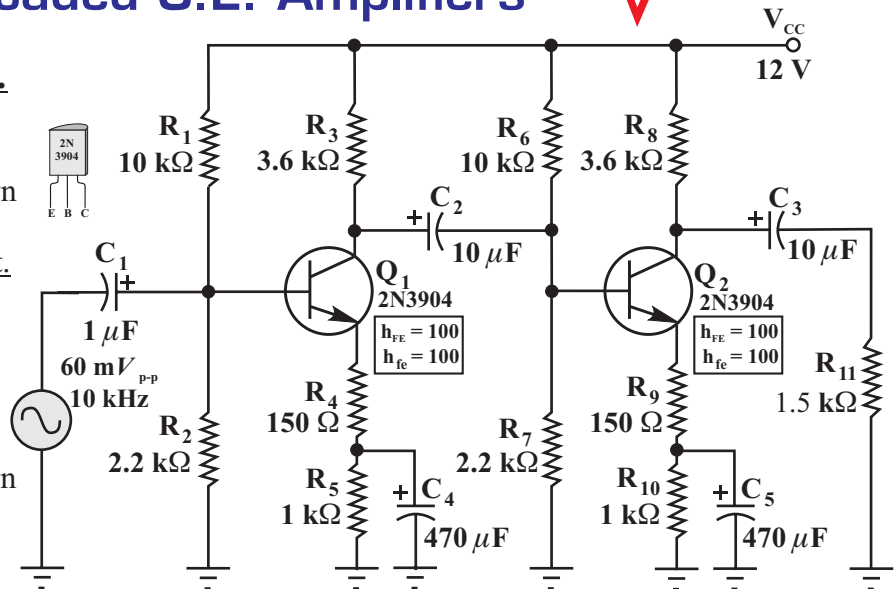


Figure 1

- 4) Using the measured values of $V_{B(Q1)}$ and $V_{C(Q1)}$, calculate $A_{V(Q1)}$. Insert this value in the measured section of Table 2. _____
- 5) Using the measured values of $V_{B(Q2)}$ and $V_{C(Q2)}$, calculate $A_{V(Q2)}$. Insert this value in the measured section of Table 2. _____
- 6) Using the measured values of $V_{B(Q1)}$ and $V_{C(Q2)}$, calculate A_{VT} . Insert this value in the measured section of Table 2. _____
- 7) Compare the values of A_{VT} (measured) vs A_{VT} (calculated). Calculate the percentage error.

$$\% \text{ Error} = \frac{|\text{measured} - \text{calculated}|}{\text{calculated}} \times 100$$


- 8) How would you account for this error? Give 3 reasons. _____

Loading Effects

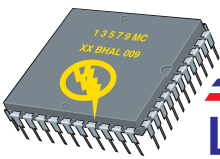- 9) Open the coupling capacitor between the first and second stage (C_2). Measure the ac voltage on the collector of stage 1. Compare this with the measured value of $V_{C(Q1)}$ that you recorded in Table 2. Explain why the value in Table 2 is lower.

$V_{C(Q1)}$ _____ (C_2 open)

$V_{C(Q1)}$ _____ measured value from Table 2



Lab 6 Cascaded C.E. Amplifiers

- 10) Replace the coupling capacitor that you removed in Question 9. Make sure that the amplifier is working normally. Connect the scope to the collector of **Stage 2**. Note the value of ac voltage and record it. It should be the same as the value you recorded in Table 2. Remove the load resistor (R_{11}). Note the value of V_{CQ2} again.

$V_{C(Q2)}$ _____ with the load resistor (R_{11}) **in** the circuit

$V_{C(Q2)}$ _____ with the load resistor (R_{11}) **out of** the circuit

Why is the ac collector voltage higher with the load resistor removed?

- 11) Make sure that the amplifier is working normally. The load resistor is in the circuit. Connect the scope to the collector of **Stage 1**. Note the value of ac voltage and record it. It should be the same as the value you recorded in Table 2. Remove the load resistor (R_{11}). Note the value of V_{CQ1} again.

$V_{C(Q1)}$ _____ with the load resistor **in** the circuit

$V_{C(Q1)}$ _____ with the load resistor **out of** the circuit

Does the addition of the load resistance (R_{11}), have an impact on the output of the first stage? _____

- 12) Based on your answer to Question 11 above, what is your opinion of the use of a second amplifier stage as a means of isolating the first stage from the load?

- 13) Remove the load resistor and replace it with an 8Ω speaker. With the generator connected with 60 mV_{p-p} applied to the input, measure the voltage that appears across the speaker. This is the same as V_{CQ2}

$V_{C(Q2)}$ _____ the voltage across the speaker.

- 14) Explain why the output is so low.

